

Lecture-1) Introduction

- * What is PE
- * Converter Types
- * Major Components
- * Applications

PE { Processing Power
I/P { electrical
O/P { electrical

DC-DC }
DC-AC } 4 combinations
AC-DC }
AC-AC }

1) Conversion among the 4 combinations

DC-DC (Solar)

AC-AC (Ceiling Fan)

EV { Battery : 300-400V
Other comps need 5-12V } DC-DC converters

2) Control : (Voltage / Current)

3) Conditioning : Switching is done { kHz, MHz
(Waveforms become rough; pulses)

V_o  actual avg.
needed

Before PE { DC-DC Conv. } \Rightarrow DC motor (E \rightarrow M) (Noisy, Slow, Huge)
 \downarrow
Generator (M \rightarrow E) (Instead: Small PE Converters)

Bigger Regulators (non-PE) \Rightarrow Used Earlier

Power gen. in Thermal } very
plants } inefficient

Renewable energy } Uses PE

Advantages:


- More efficient
- Smaller
- Faster
- Static
- Directional

Disadvantages:

- Poor Quality
- Complex

Converter Types:

AC/AC : Converter

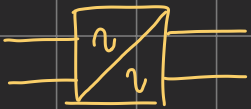

DC/AC : Inverter



DC/DC : Chopper



AC/DC : Rectifier



Motor



Choice

: PMSM

(Permanent Magnet Synchronous Machine)


Solar Power } DC

For Appliances, DC-AC Conversion

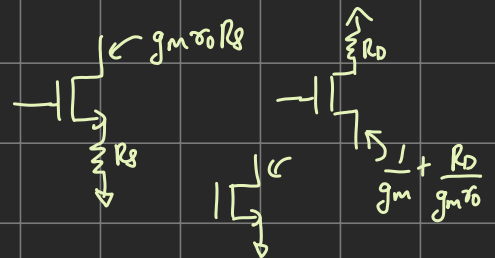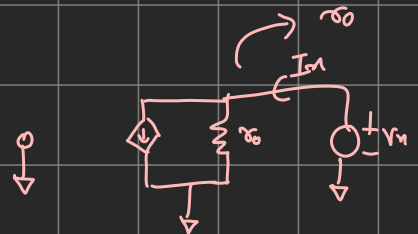

* Design system to
Convert 48V DC
to 12V DC

Voltage divider:

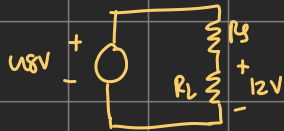

Drawbacks:

* if R_L varies,
to keep $V_o = 12V$,
 R_S needs to vary


$$\frac{u_8}{(R_S + R_L)} = I$$

$$P_{in} = \frac{(u_8)^2}{(R_S + R_L)}$$

$$P_{out} = \frac{(u_r)^2}{(R_S + R_L)^2} R_L$$

$$\frac{(u_8)^2 R_L}{(R_S + R_L)^2} \times \frac{(R_S + R_L)}{u_8^2}$$

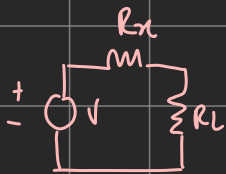
$$\Rightarrow \frac{R_L}{(R_S + R_L)} \% \text{ efficiency}$$



$$\frac{V}{(R_x + R_L)}$$

$$\begin{aligned} P_L &= V_{in} \times I_{in} \\ &= I_{in}^2 R_x \\ P_L &= \frac{V^2 R_x}{(R_x + R_L)^2} \end{aligned}$$

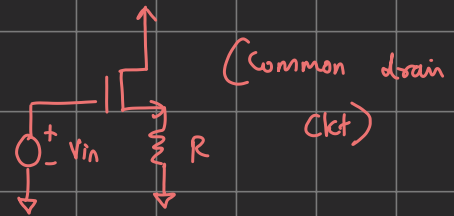$R_x \rightarrow 0, R_x \rightarrow \infty$
(can become 0)
(Switch between these; indefinitely)



Analog ckts:

— Series/shunt regulators

